

GROUP – B

(Short Answer Type Questions)

Answer any *three* of the following.

3 x 5 = 15

2. Given the logical expression $U = (A + BC)(B + \bar{C}A)$, Design the circuit using NAND gates.
3. What is race around condition? How can we overcome the race around condition?
4. Find the characteristic equation of a JK flip-flop.
5. Draw and explain the circuit of 8×1 MUX using two 4×1 MUX and one 2×1 MUX.
6. Implement the following Boolean expression using decoder:

$$F(A, B, C, D) = \prod_m(1, 2, 5, 7, 8, 10, 12, 13)$$

GROUP – C

(Long Answer Type Questions)

Answer any *three* of the following.

3 x 15 = 45

7.
 - a) What is lock out state?
 - b) Write a short note on Ring Counter.
 - c) Design Mod-6 synchronous counter using JK flip-flops and other gates. 2+5+8
8. Write short notes on any three of the following: 3x5
 - a) Johnson Counter
 - b) Propagation Delay
 - c) Parallel In Serial Out (PISO)
 - d) Even Parity Generator & Checker
 - e) Two-bit Comparator.
9.
 - a) Design a Full Adder circuit using 3:8 Decoder.
 - b) What is priority encoder? Write the truth table of 4-input priority encoder.

c) Implement the following function using 8×1 MUX:

$$F(A, B, C, D, E) = \sum_m(0, 1, 3, 4, 8, 9, 15) + \sum_d(5, 10, 13).$$

3+(2+3)+7

10. a) Find the minimal sum of product for the Boolean expression:

$$f = \sum_m(1, 3, 4, 5, 9, 10, 11) + \sum_d(6, 8) \text{ using K-map.}$$

b) Write a short note on Dual slope A/D converter.

8+7

11. a) What are the types of PLD?

b) Design a code converter circuit or BCD to Excess-3 using ROM.

c) Design a circuit which finds the square of a three-bit number using ROM.

2+6+7

=====