

2013

ELECTRIC CIRCUIT THEORY

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own words
as far as practicable.*

GROUP – A

(Multiple Choice Type Question)

1. Choose the correct alternatives for any *ten* of the following:
10 x 1 = 10
- i) Unit step function is first derivative of
- a) Ramp function b) Impulse function
c) Gate function d) Parabolic function.
- ii) A practical current source is usually represented by
- a) a resistance in series with an ideal current source
b) a resistance in parallel with an ideal current source
c) a resistance in parallel with an ideal voltage source
d) none of these.
- iii) A two-part network is defined by the relations
 $I_1 = 2V_1 + V_2$ and $I_2 = 2V_1 + 3V_2$, then Z_{12} is
- a) -2 ohm b) -1 ohm
c) $-\frac{1}{2}$ ohm d) $-\frac{1}{4}$ ohm.
- iv) The Z matrix of a 2-port network is given by
 $\begin{bmatrix} 0.9 & 0.2 \\ 0.2 & 0.6 \end{bmatrix}$. The element Y_{22} of the corresponding Y matrix of
the same network is given by
- a) 1.2 b) 0.4

6. Draw the oriented graph of a network with the fundamental cut set matrix given below:


$$Q = \begin{array}{c|ccc|ccc} & \text{Twigs} & & & \text{Links} & & \\ \hline & 1 & 2 & 3 & 4 & 5 & 6 & 7 \\ \hline & 1 & 0 & 0 & 0 & -1 & 0 & 0 \\ & 0 & 1 & 0 & 0 & 1 & 0 & 1 \\ & 0 & 0 & 1 & 0 & 0 & 1 & 1 \\ & 0 & 0 & 0 & 1 & 0 & 1 & 0 \\ \hline \end{array}$$

GROUP - C


(Long Answer Type Questions)

Answer any *three* of the following. 3 x 15 = 45

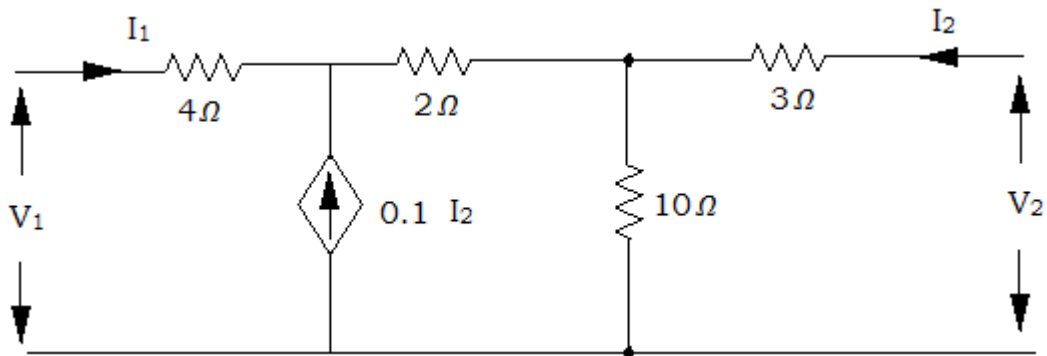7. a) What are ABCD parameters? Prove that $\Delta T = (AD - BC) = 1$. 7
- b) Find the z-parameter for the network shown in figure below. Hence find the h-parameter for the same network. 8




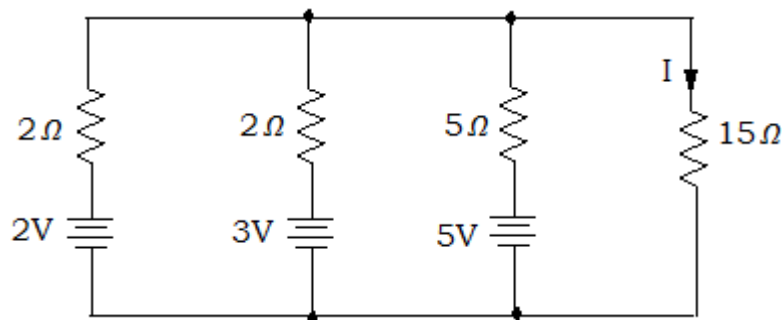8. a) State and explain Millman's theorem. Calculate the load current I in the circuit in figure by Millman's theorem.




2+6

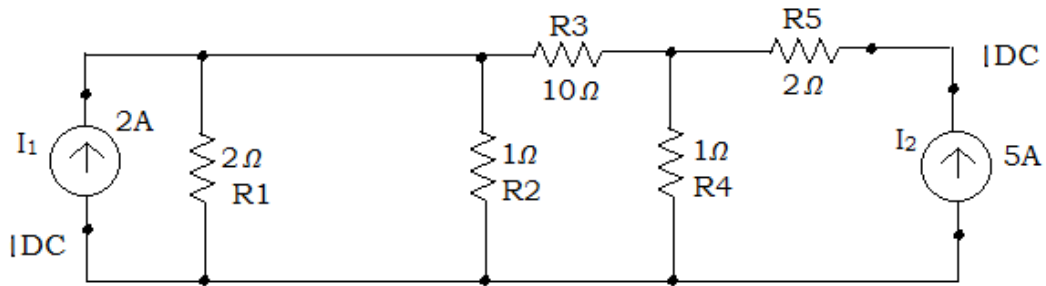- b) What is the power loss in the 10 ohm resistor? Use Thevenin's theorem in figure below: 7




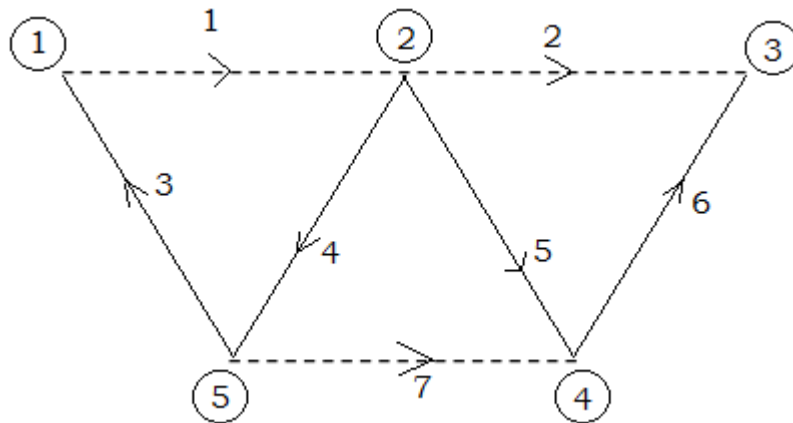9. a) What is tree? Discuss with a suitable example. 2
- b) A graph is shown in figure below. Find the tie-set and cut-set matrices and obtain the KCL & KVL equations. [bold lines indicate twigs and dotted lines the links.] 6



- c) Explain odd symmetry and even symmetry of periodic waveform. 4
10. a) Define Fourier transform. How does Fourier transform differ from Laplace transform? 5
- b) What is impulse function? Find its Laplace transform. 3

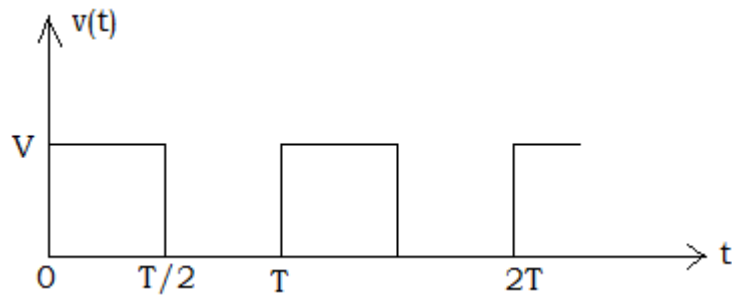- c) For the square wave shown in the figure, find the exponential Fourier series.



7

11. a) What are the advantages of active filter over passive filter? 4
- b) Design a high-pass active filter of cut-off frequency 1 kHz with a pass-band gain of 2. 5
- c) Draw the circuit diagram of a first order low-pass filter and find out the expression of the cut-off frequency. 6

=====