

CS/B.TECH (ECE-New)/SEM-4/EC-402/2012

2012

**DIGITAL ELECTRONICS AND INTEGRATED
CIRCUITS**

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own words
as far as practicable.*

GROUP – A

(Multiple Choice Type Question)

1. Choose the correct alternatives for any *ten* of the following:
10 x 1 = 10
- i) If $\sqrt{61} = 7$, the base of the number system is
- | | |
|------|------|
| a) 4 | b) 8 |
| c) 6 | d) 9 |
- ii) Which family has the better noise margin?
- | | |
|--------|--------|
| a) ECL | b) DTL |
| c) MOS | d) TTL |
- iii) The number of flip-flops required for a MOD-10 ring counter is
- | | |
|------|------------------|
| a) 4 | b) 10 |
| c) 5 | d) none o these. |
- iv) A serial adder requires
- | | |
|-------------------|---------------------|
| a) one half adder | b) two full adders |
| c) one full adder | d) one multiplexer. |

GROUP – B

(Short Answer Type Questions)

Answer any *three* of the following. 3 x 5 = 15

2. Design 16×8 memory RAM chip using two 16×4 memory RAM chips.
3. Design 5×32 decoder using 3×8 decoder and 2×4 decoder.
4. Perform conversion from D flip-flop to S-R flip-flop.
5. Design a full Subtractor using fewer
 - (i) NAND gates
 - (ii) NOR gates.
6. Explain race around condition of J-K flip-flop. Show how this condition can be avoided.

GROUP – C

(Long Answer Type Questions)

Answer any *three* of the following. 3 x 15 = 45

7. Write the definitions of BCD code and self complementing code with example. What is Gray code? What is ASCII code? Design a Gray code to binary converter using suitable logic gates.

Convert the Gray Code 11011 to equivalent binary code.
4+1+1+8+1
8. What is flip-flop? What is the difference between combinational and sequential circuits? What do you mean by the asynchronous inputs of a flip-flop? What is edge trigger flip-flop and why is it required? Convert S-R flip-flop to J-K R flip-flop. 2+2+2+3+6
9. What is ripple counter? Design a presettable 4-Bit asynchronous counter using J-K F-F. A binary ripple counter is required to count up to $(16383)_{10}$. How many F-Fs are required? If the clock frequency is 8.192 MHz, what is the frequency at the output of the MSB? 2+7+6
10. Construct a 5×32 decoder with four 3×8 Decoder and a 2×4 decoder. Show block diagram only. Describe the basic principle of successive approximation method for A/D converter.

Implement the following Boolean equations using PLA device:

a) $F1 = \sum m(0, 5, 9, 15)$

b) $F2 = \sum m(1, 3, 7, 11, 13)$

11. Write short notes on any *three* of the following:

3 x 5

a) EPROM

b) BCD to Excess-3 converter

c) R-2R Ladder type DAC

d) Even Parity Generator and Checker

e) Universal gates

f) Ring Counter.

=====