### CODE : ES 201 (Pt-I-EE)

#### CS/B.TECH (NEW)/SEM-2/ES-201 (Pt-I-EE)/2012

#### 2012

# BASIC ELECTRICAL & ELECTRONIC ENGINEERING-II (EE PART)

Full Marks: 35

The figures in the margin indicate full marks.

Candidates are required to give their answers in their own words

as far as practicable.

#### **GROUP – A**

## (Multiple Choice Type Question)

1. Choose the correct alternatives for any *five* of the following:

5 x 1 = 5

- i) In a three phase balanced system, line voltage makes an angle with phase voltages
  - a) 30° b) 60°
  - c) 90° d) 120°
- ii) The speed in which stator magnetic field rotates is called
  - a) actual speed
  - b) synchronous speed
  - c) slip speed
  - d) super-synchronous speed.
- iii) If a *d.c.* series motor is started at no load, the speed will be
  - a) rated speed
  - b) zero
  - c) very high

- d) half of the rated speed
- iv) If two static charges having magnitude 1 coulomb each are placed at 1 m apart in space, the electrostatic force developed between the charges is
  - a)  $90 \times 10^{10}$  newtons b)  $9 \times 10^{9}$  newtons
  - c)  $0.9 \times 10^9$  newtons d) 0.
- v) The regulation of a transformer is negative, if the load at the secondary side is
  - a) resistive
  - b) inductive
  - c) capacitive
  - d) combination of resistive, inductive & capacitive.
- vi) Which of the following is a four-wire system?
  - a) Delta with neutral
  - b) Star with neutral
  - c) Both delta & star
  - d) Any combination of four wires.

### **GROUP – B**

Answer any *two* of the following.

 $2 \ge 5 = 10$ 

- 2. Prove that the efficiency of transformer is maximum when iron loss is equal to copper loss.
- 3. Derive an expression for capacitance of a cylindrical capacitor, assuming grounded outer surface.
- 4. What is a three-phase balanced A.C. system? Show that, in a three-phase balanced *a.c.* circuit, the sum of current in the neutral is zero.
- 5. Derive the expression of torque of a *d.c.* series motor.

## **GROUP - C**

Answer any *two* of the following.  $2 \ge 10 = 20$ 

- 6. a) Explain the principle of operation of a transformer under loaded condition.
  - b) A 200 kVA transformer has 400 turns on the primary & 40 turns on the secondary winding. The primary is connected to 2 kV, 50 Hz supply. Find the full load, primary & secondary current, secondary *emf* & the maximum flux in the core. Neglect leakage drop & no-load primary current.
- 7. a) Explain the open characteristics (OCC) of a DC generator.
  - b) An 8-pole, 400 V shunt motor has 960 wave connected armature conductors. The full load armature current is 40 A & flux per pole is 0.02 Wb. The armature resistance is 0.1  $\Omega$  and the contact drop is 1 V per brush. Calculate the full load speed of the motor.
  - c) Why starter is needed to start a *d.c.* motor? 2+6+2
- 8. a) A three-phase induction motor is self-starting. Explain.
  - b) Obtain the relation between the slip and frequency of the rotor induced *emf*.
  - c) A 4-pole, 3-phase, 275 kW, 440 V, 50 Hz induction motor is running with a slip of 4%. Find
    - i) synchronous speed
    - ii) rotor speed
    - iii) frequency of the rotor induced *emf*. 3+2+5
- 9. a) Explain the principle of measurement of balanced 3phase power by 2-Wattmeter method. Draw the neat circuit & phasor diagrams.

- b) These equal impedances (6+j8) Ω are connected across a 400 V, 3-phase, 50 Hz supple. Calculate –
- i) The line current & the phase current
- ii) power factor
- iii) active & reactive drawn by load per phase. 5+5

\_\_\_\_\_

## ES-201 (Pt-II-ECE)

### CS/B.TECH (NEW)/SEM-2/ES-201 (Pt-II-ECE)/2012

### 2012

# BASIC ELECTRICAL & ELECTRONIC ENGINEERING-II (ECE PART)

Full Marks: 35

The figures in the margin indicate full marks.

Candidates are required to give their answers in their own words

as far as practicable.

# **GROUP – A**

# (Multiple Choice Type Question)

1. Choose the correct alternatives for any *five* of the following:

5 x 1 = 5

- i) An ideal Op-Amp is an ideal
  - a) voltage controlled current source
  - b) voltage controlled voltage source
  - c) current controlled current source
  - d) current controlled voltage source
- ii) The AND function can be realized by using only n number of NOR gates. What is n equal to?
  - a) 2 b) 3

- c) 4 d) 5
- iii) The Boolean expression  $ABC + \overline{ABC} + AB\overline{C} + \overline{ABC}$  is of
  - a) OR gate b) AND gate
  - c) EX-NOR gate d) EX-OR gate
- iv) Which of the following statements is/are correct in regard to excess 3 code?
  - a) It is a BCD code
  - b) It is an unweighter code
  - c) It is a self complementing code
  - d) All of these.
- v) In Barkhausen criterion, phase of  $A\beta$  is
  - a) 0°
  - b) multiple of 180°
  - c) 0° or multiple of 180°
  - d) 0° or multiple of 360°
- vi) In intverting amplifier circuit if input & feedback resistances are 1 k $\Omega$  ans 3 k $\Omega$ , respectively, i/p voltages is 3 volte and power supply voltage is  $\pm$  6V, then the output voltage of Op-Amp is
  - a) -6 volt b) +6 volte
  - c) -9 volt d) +9 volt

#### **GROUP – B**

Answer any *two* of the following.  $2 \ge 5 = 15$ 

- 2. Mention the advantages and disadvantages of negative feedback amplifier.
- 3. Discuss the operation of op-amp as an integrator.
- 4. a) Implement the function  $F = \overline{(AB + CD)}$  using NAND gates.
  - b)  $(11011)_2 = (?)_{10}$

- c) Write down the basic difference between enhancement type and depletion type MOSFETs. 2+2+1
- 5. a) What is virtual ground of an Op-Amp?
  - b) Draw and explain the voltage comparator circuit using Op-Amp. 2+3

#### **GROUP – C**

## (Long Answer Type Questions)

Answer any *three* of the following.  $2 \ge 10 = 20$ 

- 6. a) What is the effect of negative feedback on output impedance and phase distortion?
  - b) An amplifier has a voltage gain of -100. The feedback ratio is -0.04. Find
    - i) the voltage gain with feedback
    - ii) the amount of feedback in dB
    - iii) the output voltage of the feedback amplifier for an input voltage of 40 mV
    - iv) the feedback factor
    - v) the feedback voltage.
- 7. a) Explain the basic operation of depletion type *n* channel MOSFET with a suitable diagram.
  - b) What are the basic differences between BJT and FET?
  - c) As  $V_{GS}$  is changed from 0 V to 0.2 V keeping  $V_{DS}$  constant,  $I_D$  of the FET drops from 10.25 mA to 9.56 mA. What is the transconductance of the FET? If the a.c. drain resistance is 32 k $\Omega$ , find the amplification factor of the FET.
  - d) What do you mean by pinch off voltage for n-channel JFET? 4+2+2+2

8. a) If the feedback resistance  $R_f$  is replaced by a diode for a negative feedback amplifier using Op-Amp, then derive the expression of o/p voltage  $v_o$  for it. Also mention the type of application for this modification. 4+1



b) For the given circuit find the output voltage  $v_o$ .



11. Write short notes on any *two* of the following:

- a) Topologies of feedback amplifier
- b) Summing amplifier
- c) CMOS
- d) Design og exclusive-OR gate.

\_\_\_\_\_